


Homework #2
CMPE-12L

James Vrionis
J.Vrionis@cs.cmu.edu
1562232
CMPE 12/L
1-24-17



(5 pts) Build a 5-input AND gate out of 2-input AND gates.

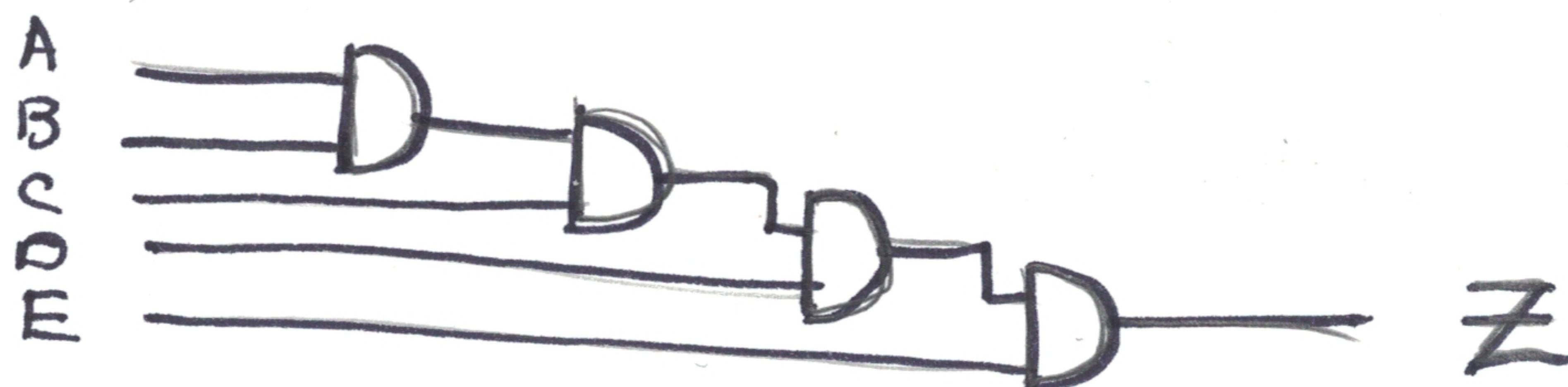ANSWER: Using the fact that AND is an associative logical operator, that means for some output $Z = (((A \text{ AND } B) \text{ AND } C) \text{ AND } D) \text{ AND } E$ with inputs A,B,C,D and E.



$$\therefore (((((A \cdot B) \cdot C) \cdot D) \cdot E)$$

(5 pts) How many output lines will a five-input decoder have?

ANSWER: A decoder takes its inputs and converts to a "one-hot" output. With the inputs, you are selecting which output is asserted. The number of outputs in a decoder is equal to 2^n with n equal to the number of inputs. Therefore, a five-input decoder would have 32 outputs.


(5 pts) How many output lines will a 16-input multiplexer have? How many select lines will this multiplexer have?

ANSWER: A multiplexer selects one of many inputs and presents it on the output. There is one output in a multiplexer. The number of select lines necessary in a multiplexer is \log_2 of the number of inputs. 1 select line can select between 2 inputs, 2 can select between 4 inputs, 3 can select between 8, and 4 can select from 16. Thus, this multiplexer will have 4 select lines.

(5 pts) You know a byte is 8 bits. We call a 4-bit quantity a nibble. If a byte-addressable memory has a 14-bit address, how many nibbles of storage are in this memory?


ANSWER: $= 2^{14} \because 14\text{-bit address means that you can address } 2^{14}$
 $= 2 * 2^{14} \because \text{Each memory location contains 1 byte, equal to two nibbles.}$
 $= 2^{15} \because 2^{15} = 2 * 2^{14}$
 $= 32868 \text{ nibbles of storage in this memory.}$

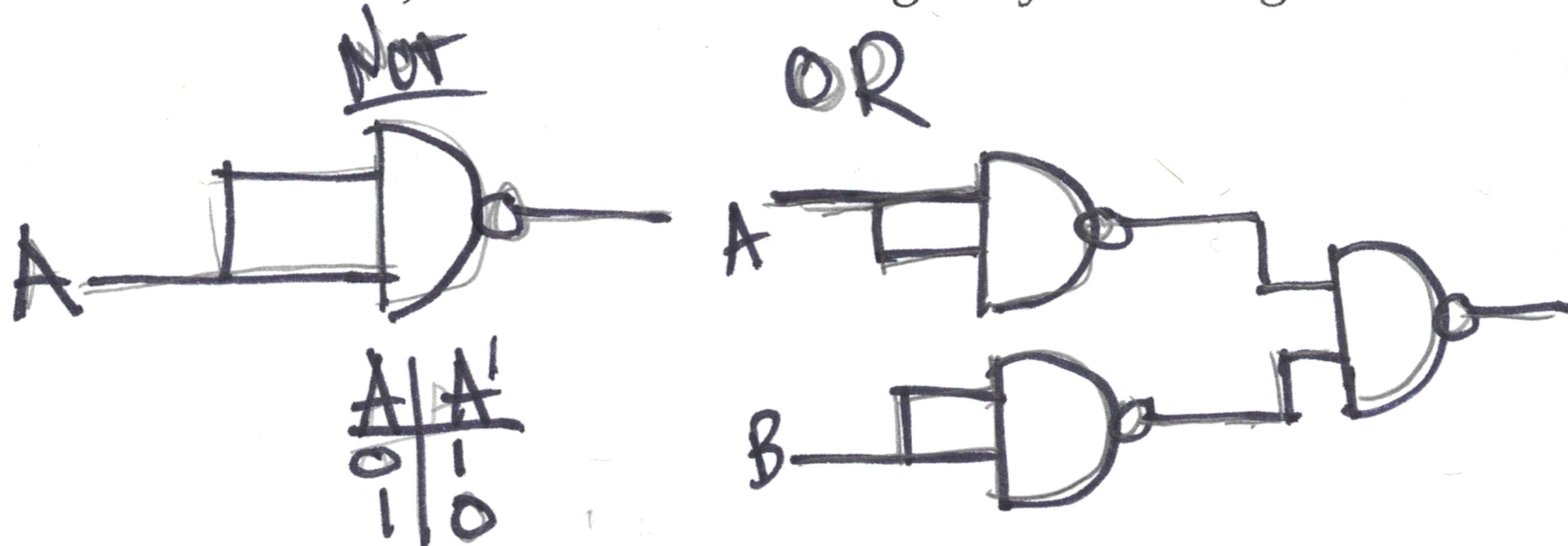(15 pts) All logic circuits can be created by NAND gates. Prove this by building logic circuits for NOT, OR and AND using only NAND gates.



AB	A'	B'	AB'	$(A \cdot B)'$	$A+B$
00	1	1	1	0	0
01	1	0	0	1	1
10	0	1	0	1	1
11	0	0	0	0	1

Q4

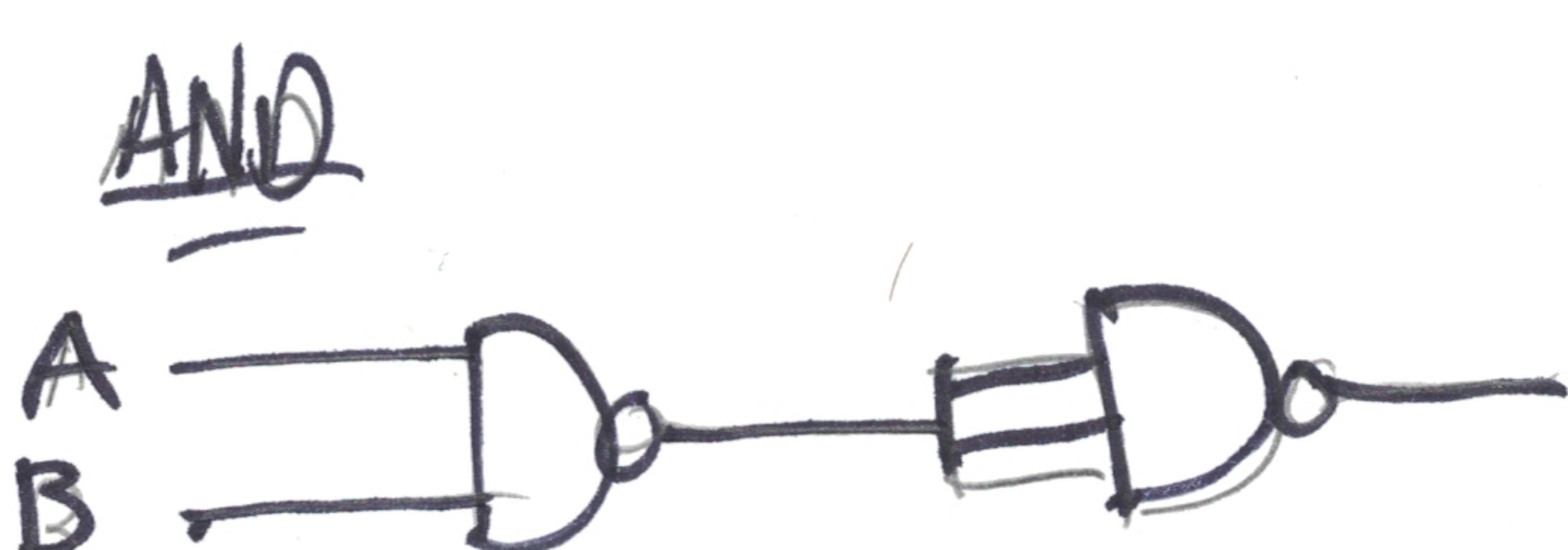


AB	A'	B'	$(A \cdot B)'$	$((A \cdot B)')'$
00	0	1	1	0
01	0	0	0	1
10	1	0	0	1
11	0	0	0	1

Q5

(10 pts) Distinguish between a memory address and the memory's addressability.

Answer: Memory's addressability is the way in which a computer identifies memory locations. The width of the address bus determines how many memory locations can be addressed. For example: 1 bit address bus = 2 memory locations, 2 bit address bus = 3 memory locations, 3 bit address bus = 8 memory locations, and so on. Addressable memory can be calculated using the number of storage locations * size of each storage location.

 (15 pts) Give the logic circuit below, fill in the truth table for the output value Y.



A	B	C	$(A \cdot B)$	$(A \cdot B)'$	$(B+C)$	$(B+C)'$	(1)	(2)	(3)	(4)	y = output
0	0	0	0	1	0	1	1	1	0	0	0
0	0	1	0	1	1	0	0	1	0	0	0
0	1	0	0	1	1	0	0	1	0	0	0
0	1	1	0	1	1	0	0	1	0	0	0
1	0	0	0	1	0	1	1	1	0	0	0
1	0	1	0	1	1	0	0	1	0	0	0
1	1	0	0	0	1	0	0	0	1	0	0
1	1	1	0	0	1	0	0	0	1	0	0

$$[(B+C)' \cdot (A \cdot B)'] = (1)$$

$$[(B+C)' \cdot (A \cdot B)'] + (A \cdot B)' = (2)$$

$$[(B+C)' \cdot (A \cdot B)'] + (A \cdot B)' = (3)$$


$$[(B+C)' \cdot (A \cdot B)'] \cdot [(B+C)' \cdot (A \cdot B)'] + (A \cdot B)' = (1) \cdot (3) = (4)$$

since the output $y = (4)$, y is a column of all zeros.

Q10

(15 pts) Create the Logic gates for the truth Table below.

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

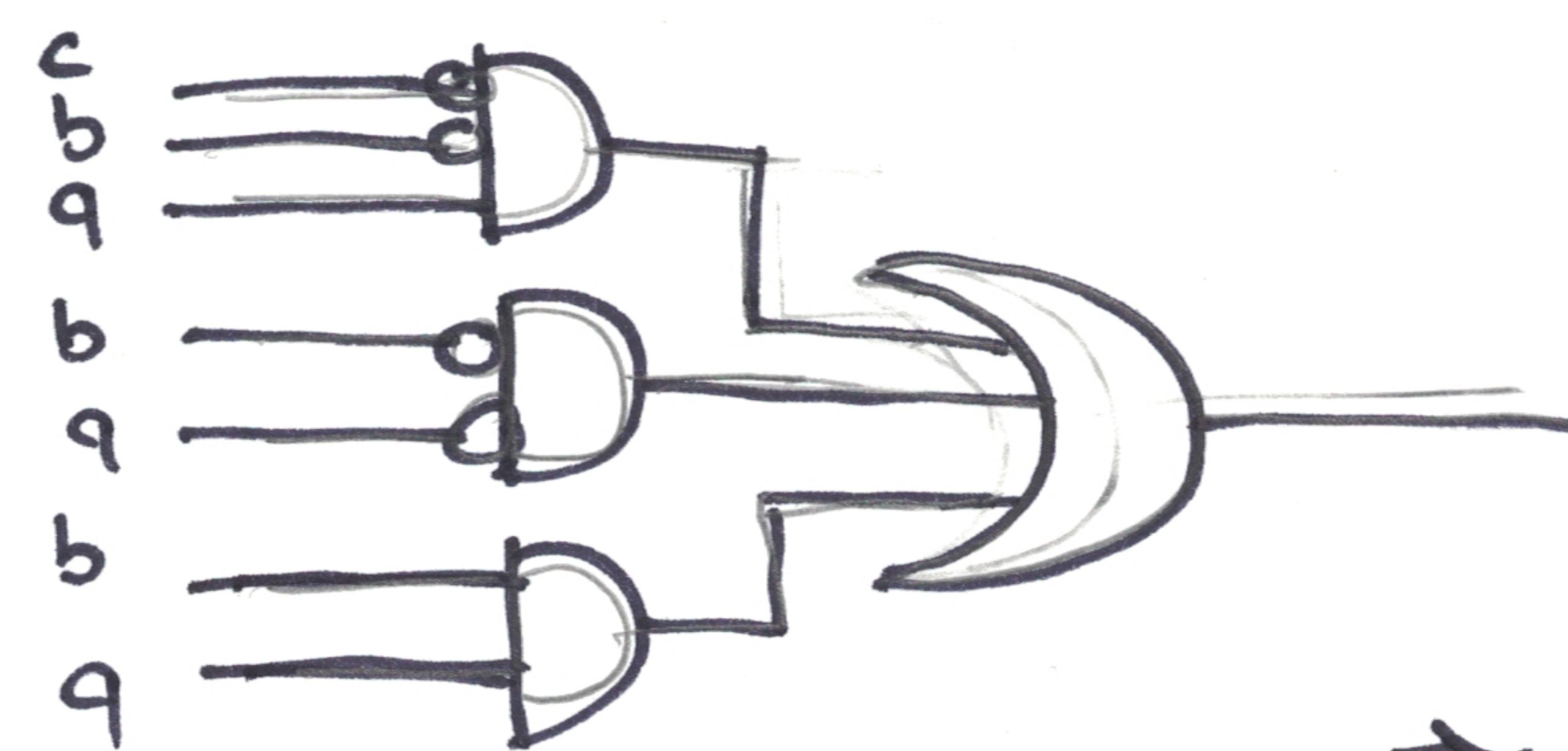

$$\begin{aligned}
 & a'b'c' + a'b'c + ab'c' + abc \\
 \Rightarrow & a'b'(c+c') + ab(c(c')) + ab \\
 \therefore & a'b' + ab + ab'c' \quad \boxed{24}
 \end{aligned}$$

(25 pts) Convert the following numbers to binary and perform binary subtraction on them. Do not use additive inverse.

- a. $39 - 22 \Rightarrow 00100111 - 00010110 \Rightarrow 00010001 \Rightarrow 17$
- b. $25 - 14 \Rightarrow 00011001 - 00001110 \Rightarrow 00001011 \Rightarrow 11$
- c. $39 - 12 \Rightarrow 00100111 - 00001100 \Rightarrow 00011011 \Rightarrow 27$
- d. $18 - 11 \Rightarrow 00010010 - 00001011 \Rightarrow 0000111 \Rightarrow 7$
- e. $30 - 26 \Rightarrow 00011110 - 00011010 \Rightarrow 00000100 \Rightarrow 4$

$$\begin{array}{r}
 a. \quad \cancel{0} \cancel{0} \cancel{1} \cancel{0} \cancel{0} \cancel{1} \cancel{1} \\
 - \cancel{0} \cancel{0} \cancel{0} \cancel{1} \cancel{0} \cancel{1} \cancel{0} \\
 \hline
 00010001 \checkmark
 \end{array}$$

$$\begin{array}{r}
 b. \quad \cancel{0} \cancel{0} \cancel{0} \cancel{1} \cancel{1} \cancel{0} \cancel{1} \\
 - \cancel{0} \cancel{0} \cancel{0} \cancel{0} \cancel{1} \cancel{1} \cancel{0} \\
 \hline
 00001011 \checkmark
 \end{array}$$

$$\begin{array}{r}
 c. \quad \cancel{0} \cancel{0} \cancel{1} \cancel{0} \cancel{0} \cancel{1} \cancel{1} \\
 - \cancel{0} \cancel{0} \cancel{0} \cancel{1} \cancel{1} \cancel{0} \cancel{0} \\
 \hline
 00011011 \checkmark
 \end{array}$$

$$\begin{array}{r}
 d. \quad \cancel{0} \cancel{0} \cancel{0} \cancel{1} \cancel{0} \cancel{0} \cancel{1} \cancel{0} \\
 - \cancel{0} \cancel{0} \cancel{0} \cancel{0} \cancel{1} \cancel{0} \cancel{1} \\
 \hline
 00000111 \checkmark
 \end{array}$$

$$\begin{array}{r}
 e. \quad 00011110 \\
 - 00011010 \\
 \hline
 00000100 \checkmark
 \end{array}$$